


# Home Work 11

11-1 Using the loop rule, derive the differential equation for an  $LC$  circuit:

$$L \frac{d^2 q}{dt^2} + \frac{1}{C} q = 0$$

11-2 A series circuit containing inductance  $L_1$  and capacitance  $C_1$  oscillates at angular frequency  $\omega$ . A second series circuit, containing inductance  $L_2$  and capacitance  $C_2$ , oscillates at the same angular frequency. In terms of  $\omega$ , what is the angular frequency of oscillation of a series circuit containing all four of these elements? Neglect resistance. (*Hint*: Use the formulas for equivalent capacitance and equivalent inductance; see Section [25-4](#) and Problem [47](#) in Chapter [30](#).)

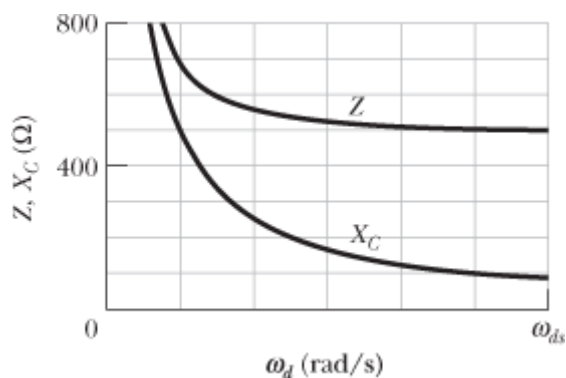11-3 An alternating source with a variable frequency, a capacitor with capacitance  $C$ , and a resistor with resistance  $R$  are connected in series. The following figure gives the impedance  $Z$  of the circuit versus the driving angular frequency  $\omega_d$ ; the curve reaches an asymptote of  $500 \Omega$ , and the horizontal scale is set by  $\omega_{ds} = 300 \text{ rad/s}$ . The figure also gives the reactance  $X_C$  for the capacitor versus  $\omega_d$ . What are (a)  $R$  and (b)  $C$ ?



11-4 An alternating source with a variable frequency, an inductor with inductance  $L$ , and a resistor with resistance  $R$  are connected in series. The following figure gives the impedance  $Z$  of the circuit versus the driving angular frequency  $\omega_d$ , with the horizontal axis scale set by  $\omega_{ds} = 1600 \text{ rad/s}$ . The figure also gives the reactance  $X_L$  for the inductor versus  $\omega_d$ . What are (a)  $R$  and (b)  $L$ ?

